

CADD -- JOB ASSIGNMENT

Experiential Learning: Level 1- Banana Problem statement

1. Problem Statement: 8-bit BCD Adder

Design hardware to add two 8-bit unsigned BCD numbers. Sketch a schematic for your design, and write an HDL module for the BCD adder. The inputs are A, B, and Cin, and the outputs are S and Cout. Cin and Cout are 1-bit carries, and A, B, and S are 8-bit BCD numbers.

CODE

```
module banana1 (
    input logic [7:0] A, B,
    input Cin,
    output [7:0] S,
    output Carry
);
    wire [3:0] lower_sum, upper_sum;
    wire lower_carry, upper_carry;
    wire [3:0] lower_corrected, upper_corrected;
    wire lower_overflow, upper_overflow;


    assign {lower_carry, lower_sum} = A[3:0] + B[3:0] + Cin;
    assign lower_overflow = (lower_sum > 4'd9) ? 1'b1 : 1'b0;
    assign lower_corrected = lower_overflow ? lower_sum + 4'd6 : lower_sum;
    assign {upper_carry, upper_sum} = A[7:4] + B[7:4] + lower_overflow;
    assign upper_overflow = (upper_sum > 4'd9) ? 1'b1 : 1'b0;
    assign upper_corrected = upper_overflow ? upper_sum + 4'd6 : upper_sum;
    assign S = {upper_corrected, lower_corrected};
    assign Carry = upper_carry | upper_overflow;
endmodule
```

TESTBENCH


```
module banana1tb;
    reg [7:0] A, B;
    reg Carry_in;
    wire [7:0] Sum;
    wire Carry_out;

    banana1 dut (
        A,
        B,
        Carry_in,
        Sum,
        Carry_out
    );
    initial begin
        A = 8'b00000010; B = 8'b00000011; Carry_in = 0; #10;
        A = 8'b00001001; B = 8'b00000010; Carry_in = 0; #10;
        A = 8'b01011000; B = 8'b01001001; Carry_in = 0; #10;
        A = 8'b00000101; B = 8'b00000101; Carry_in = 1; #10;
        A = 8'b10011001; B = 8'b10011001; Carry_in = 0; #10;
        A = 8'b00000000; B = 8'b00000000; Carry_in = 0; #10;
        A = 8'b00100110; B = 8'b00010101; Carry_in = 1; #10;
    end
endmodule
```

RTL

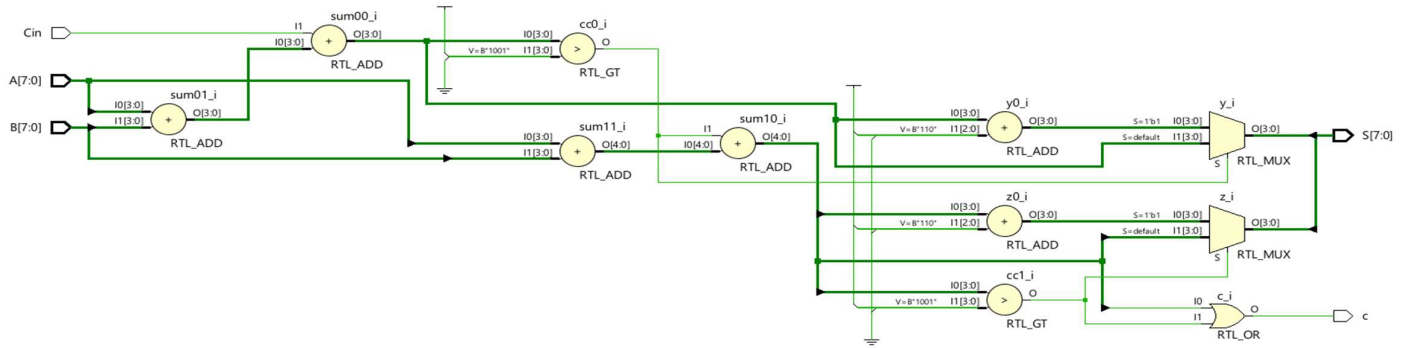


Technology schematic

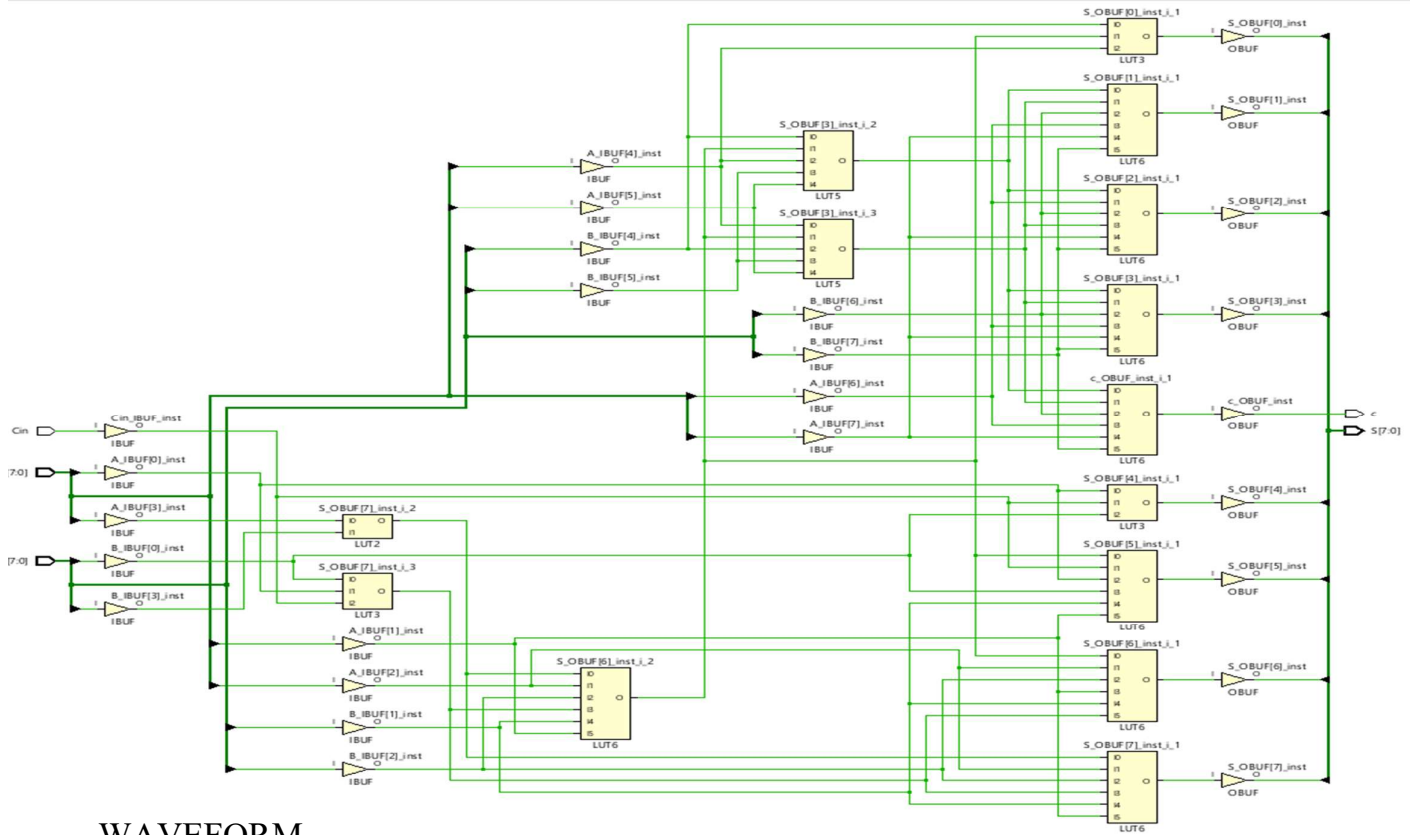

WAVEFORM



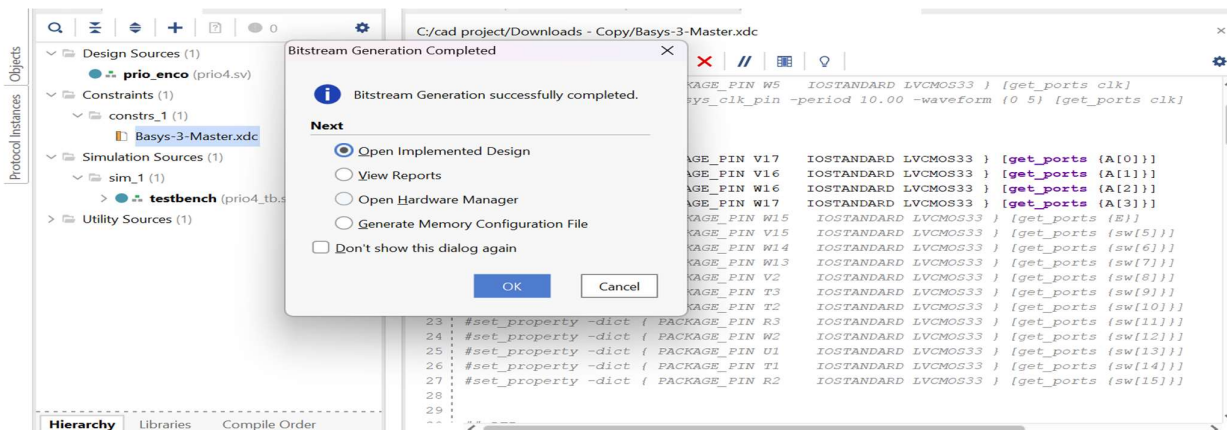

2. Problem Statement: FPGA Flow – Combinational & Sequential circuits

How many ARTY 100T FPGA CLBs/recourses are required to perform each of the following functions? Show how to configure one or more CLBs to perform the function.

- You should be able to do this by inspection, without performing logic synthesis.
- Write HDL module, perform synthesis, and tabulate the synthesis results

(a) The combinational function

$$Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C\overline{D} + \overline{A}BD + \overline{A}B\overline{C}\overline{D} + \overline{B}\overline{C}\overline{D} + \overline{A}$$

CODE

```
module banana_2 (
    input logic InputA, InputB, InputC, InputD,
    output logic OutputY
);
    assign OutputY = ~InputA |
        (InputA & InputB & InputD) |
        (InputA & InputC & ~InputD) |
        (InputA & ~InputB & ~InputC);
endmodule
```

TESTBENCH

```
module banana_21tb;
    reg InputA, InputB, InputC, InputD;
    wire OutputY;


    banana_21 dut (
        InputA,
        InputB,
        InputC,
        InputD,
        OutputY
    );
    initial begin
        #20; InputA = 0; InputB = 0; InputC = 0; InputD = 0;
        #10; InputA = 0; InputB = 0; InputC = 0; InputD = 1;
        #10; InputA = 0; InputB = 0; InputC = 1; InputD = 0;
        #10; InputA = 0; InputB = 0; InputC = 1; InputD = 1;
        #10; InputA = 0; InputB = 1; InputC = 0; InputD = 0;
        #10; InputA = 0; InputB = 1; InputC = 0; InputD = 1;
        #10; InputA = 0; InputB = 1; InputC = 1; InputD = 0;
        #10; InputA = 0; InputB = 1; InputC = 1; InputD = 1;
        #10; InputA = 1; InputB = 0; InputC = 0; InputD = 0;
        #10; InputA = 1; InputB = 0; InputC = 0; InputD = 1;
        #10; InputA = 1; InputB = 0; InputC = 1; InputD = 0;
        #10; InputA = 1; InputB = 0; InputC = 1; InputD = 1;
    end
```

```


#10; InputA = 1; InputB = 1; InputC = 0; InputD = 0;
#10; InputA = 1; InputB = 1; InputC = 0; InputD = 1;
#10; InputA = 1; InputB = 1; InputC = 1; InputD = 0;
#10; InputA = 1; InputB = 1; InputC = 1; InputD = 1;
end
endmodule

```


WAVEFORM

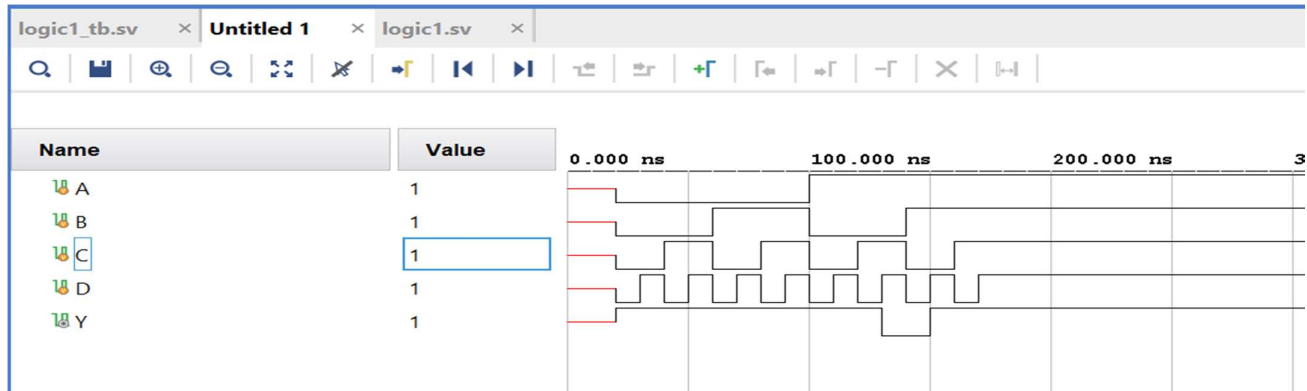


RTL

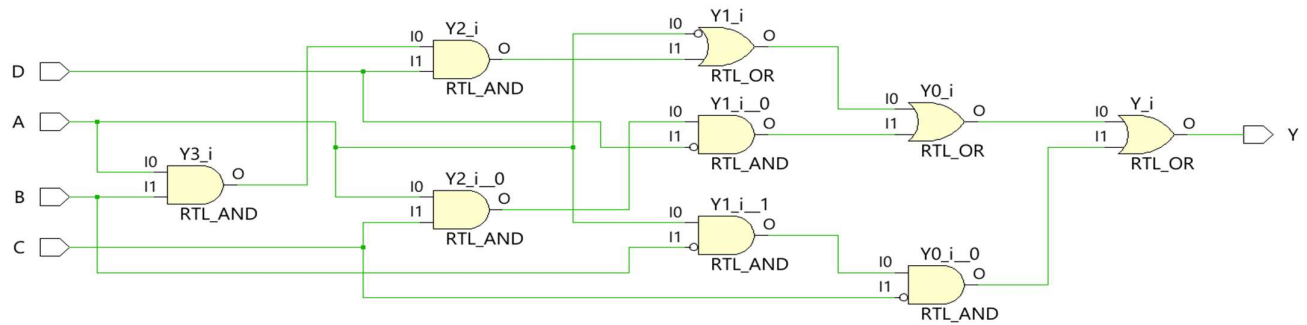

Technology schematic

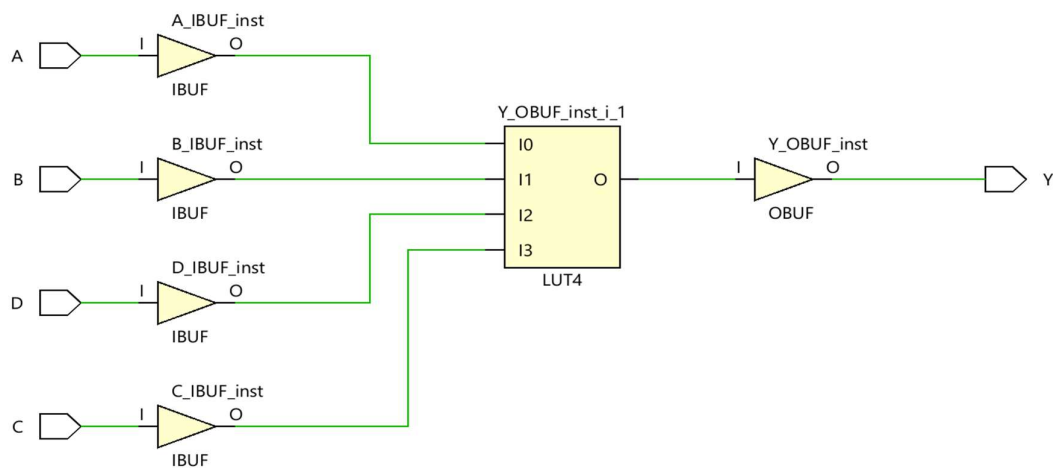

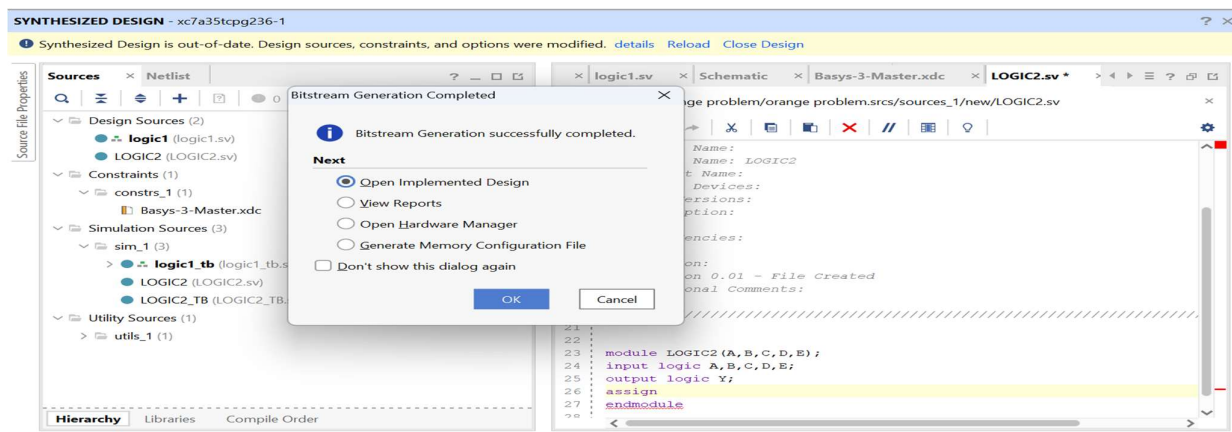

(b) The combinational function

$$Y = ABC + ABD + ABE + ACD + ACE + \overline{(A + D + E)} + \overline{BCD} + \overline{BCE} + \overline{BDE} + \overline{CDE}$$


CODE

```
module banana_22(A,B,C,D,E,Y);
input logic A,B,C,D,E;
output logic Y;
assign Y=( A&B&C | A&B&D | A&B&E | A&C&D | A&C&E | ~(A|B|E) | ~B&~C&D | ~B&~C&E | ~B&~D&~E | ~C&~D&~E );
endmodule
```


TESTBENCH

```
module banana_22tb;
reg A,B,C,D,E;
wire Y;
banana_22 dut(A,B,C,D,E,Y);
initial
begin
#10;A=0;B=0;C=0;D=0;E=0;
#10;A=0;B=0;C=0;D=0;E=1;
#10;A=0;B=0;C=0;D=1;E=0;
#10;A=0;B=0;C=0;D=1;E=1;
end
endmodule
```

WAVEFORM

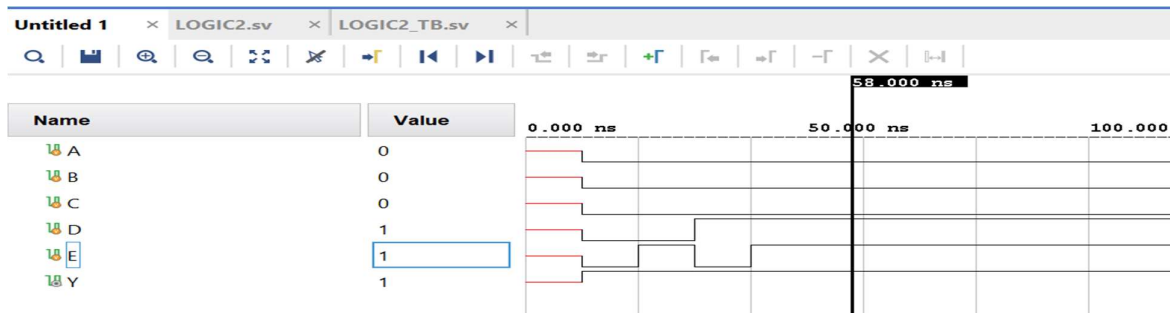

RTL

 


CODE

```
module banana_23(A,B,C,D,Y,Z);
input logic A,B,C,D;
output logic Y,Z;
assign Y= ( ~A&D | A&~C&D | A&~B&C | A&B&C&D );
assign Z= ( B&D | A&~C&D );
endmodule
```


TESTBENCH

```
module banana_23tb;
reg A,B,C,D;
wire Y,Z;
banana_23 dut(A,B,C,D,Y,Z);
initial
begin
#20;A=0;B=0;C=0;D=0;
#10;A=0;B=0;C=0;D=1;
#10;A=0;B=0;C=1;D=0;
#10;A=0;B=0;C=1;D=1;
#10;A=0;B=1;C=0;D=0;
#10;A=0;B=1;C=0;D=1;
#10;A=0;B=1;C=1;D=0;
#10;A=0;B=1;C=1;D=1;
#10;A=1;B=0;C=0;D=0;
#10;A=1;B=0;C=0;D=1;
#10;A=1;B=0;C=1;D=0;
#10;A=1;B=0;C=1;D=1;
#10;A=1;B=1;C=0;D=0;
#10;A=1;B=1;C=0;D=1;
#10;A=1;B=1;C=1;D=0;
#10;A=1;B=1;C=1;D=1;
end
endmodule
```


WAVEFORM

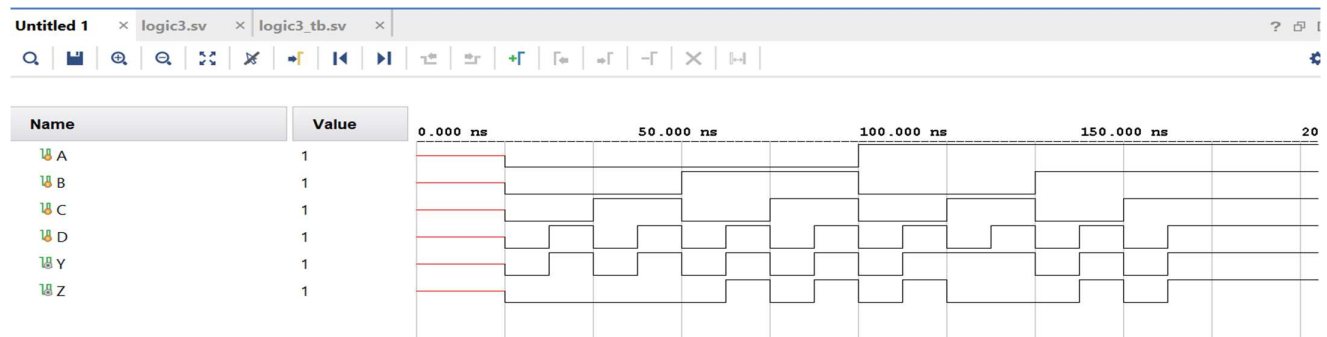

RTL

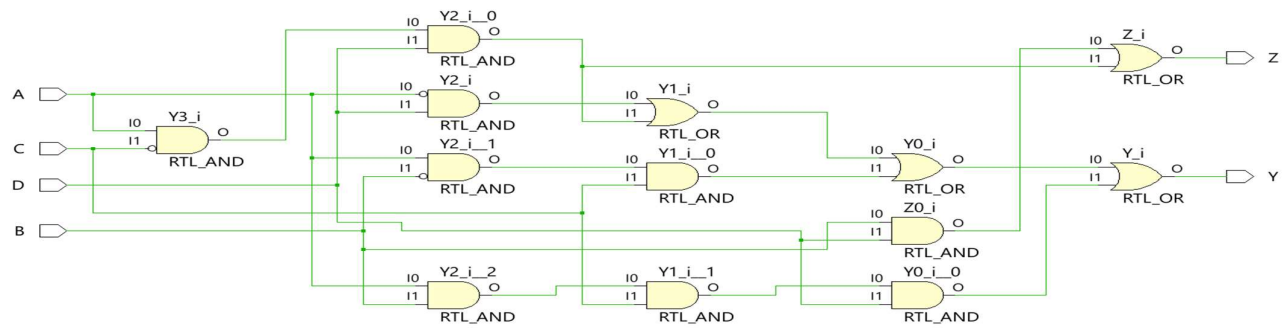

Technology schematic

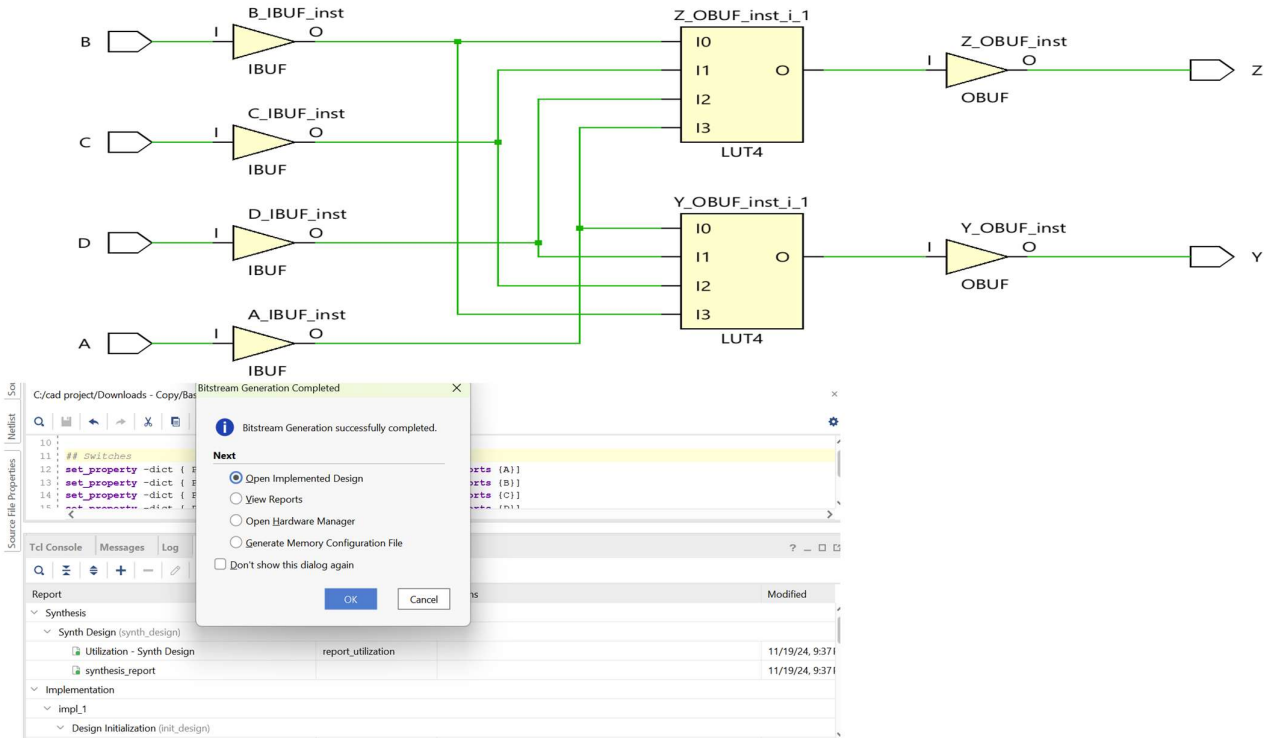

(d) The function from –

A circuit has four inputs and two outputs. The inputs, A3:0, represent a number from 0 to 15. Output P should be TRUE if the number is prime (0 and 1 are not prime, but 2, 3, 5, and so on, are prime). Output D should be TRUE if the number is divisible by 3. Give simplified Boolean equations for each output and sketch a circuit.


CODE

```
module banana_24(
    input logic [3:0] A,
    output logic P,D
);
    assign P =
        ((!A[3]&(!A[2]&A[1]&(!A[0])))((!A[3]&(!A[2])&A[1]&A[0]))((!A[3]&A[2]&(!A[1])&A[0]))((!A[3]&A[2]&A[1]&A[0]))(A[3]&(!A[2])&A[1]&A[0]))(A[3]&A[2]&(!A[1])&A[0]);
    assign
        D=((!A[3]&(!A[2]&(!A[1]&(!A[0])))((!A[3]&(!A[2])&A[1]&A[0]))((!A[3]&A[2]&A[1]&(!A[0]))(A[3]&(!A[2])&(!A[1])&A[0]))(A[3]&A[2]&(!A[1])&(!A[0]))(A[3]&A[2]&A[1]&A[0]));
endmodule
```



TESTBENCH

```
module banana_24tb;
  reg [3:0] A;
  wire P, D;
  banana_24 dut (A,P,D);
  initial
  begin
    A = 4'd0; #10;
    A = 4'd1; #10;
    A = 4'd2; #10;
    A = 4'd3; #10;
    A = 4'd4; #10;
    A = 4'd5; #10;
    A = 4'd6; #10;
    A = 4'd7; #10;
    A = 4'd8; #10;
    A = 4'd9; #10;
    A = 4'd10; #10;
    A = 4'd11; #10;
    A = 4'd12; #10;
    A = 4'd13; #10;
    A = 4'd14; #10;
    A = 4'd15; #10;
  end
endmodule
```


WAVEFORM

 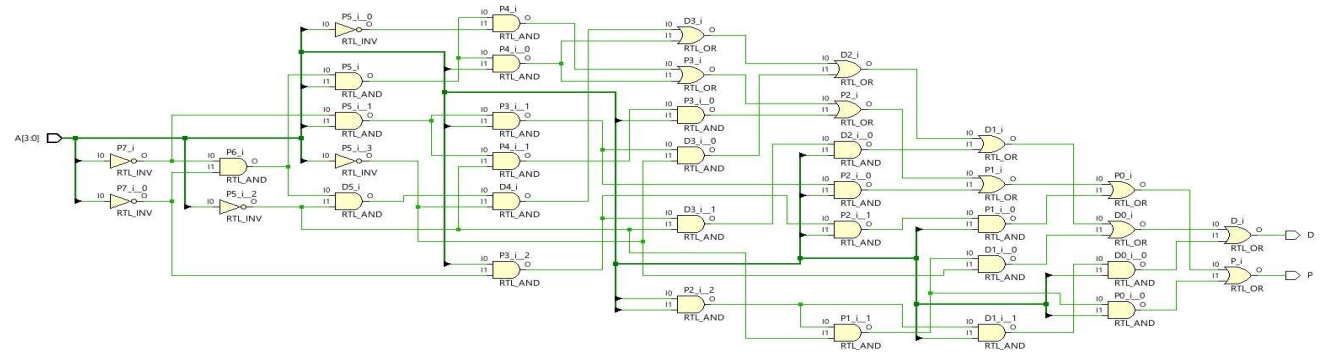

RTL



Technology schematic

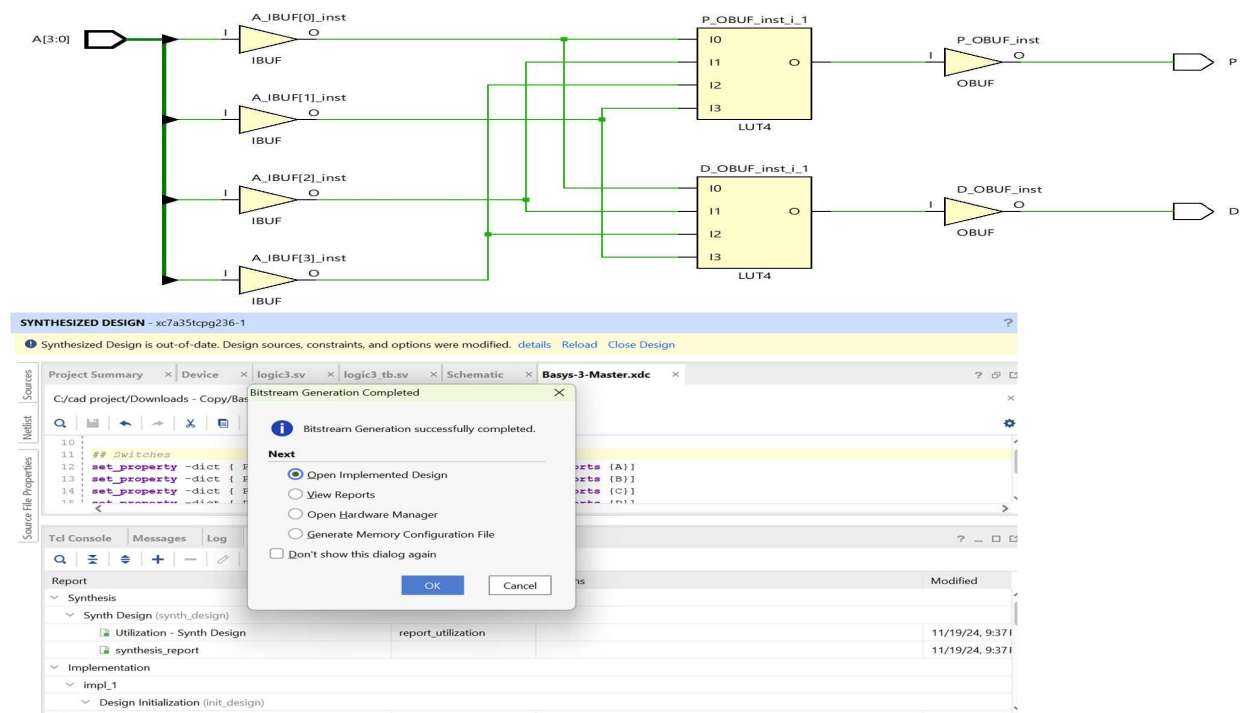

(e) A four-input priority encoder

CODE

```
module banana_25(input logic [3:0] A, output logic [1:0] Y, output logic valid);
  always_comb
  casez(A)
    4'b0001, 4'b001x, 4'b01xx, 4'b1xxx : Y = 2'b00;
    4'b0010, 4'b0011, 4'b01xx, 4'b1xxx : Y = 2'b01;
    4'b0100, 4'b0101, 4'b01xx, 4'b1xxx : Y = 2'b10;
    4'b1000, 4'b1001, 4'b10xx, 4'b1xxx : Y = 2'b11;
    default : Y = 2'b00;
  endcase
  assign valid = (A != 4'b0000);
endmodule
```


TESTBENCH

```
module job_q_2.5_tb;
  reg [3:0] A;
  wire [1:0] Y;
  wire valid;


  job_q_2.5 DUT (A, Y, valid);

  initial begin
    A = 4'b0000; #10;
    A = 4'b0001; #10;
    A = 4'b0010; #10;
    A = 4'b0100; #10;
    A = 4'b1000; #10;
    A = 4'b1100; #10;
    A = 4'b1110; #10;
    A = 4'b1111; #10;
  end
endmodule
```



WAVEFORM

 

RTL

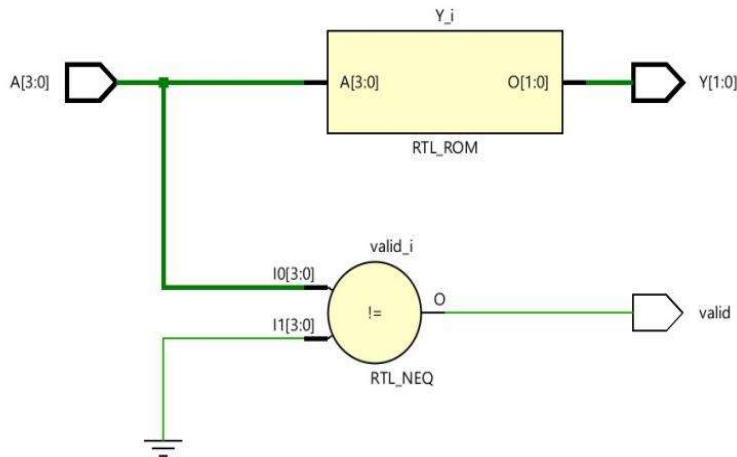

Technology schematic

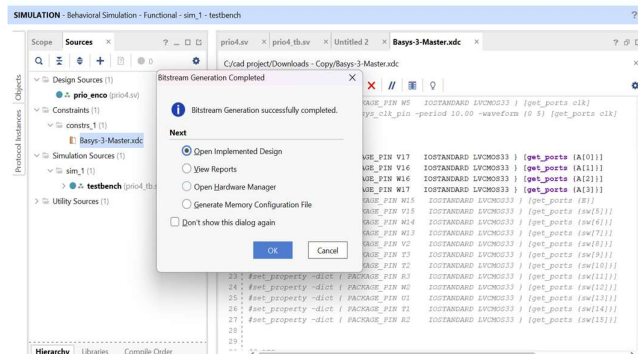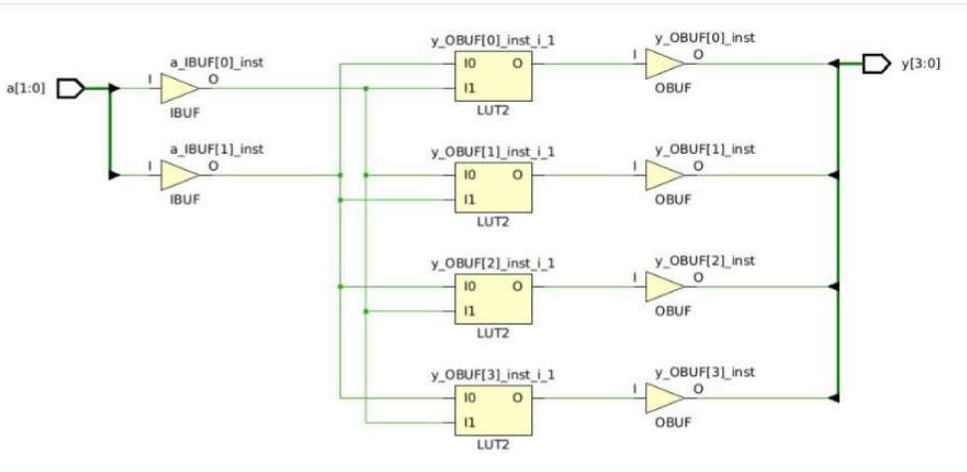

(f) An eight-input priority encoder

CODE

```
module banana_26(
  input logic [7:0] A,
  output logic [2:0] Y
);
  always_comb begin
```

```

casez (A)
  8'b00000001, 8'b0000001x, 8'b000001xx, 8'b00001xxx, 8'b0001xxxx, 8'b001xxxxx, 8'b01xxxxxx, 8'b1xxxxxxx: Y = 3'b000;
  8'b00000010, 8'b0000011x, 8'b00001xxx, 8'b0001xxxx, 8'b001xxxxx, 8'b01xxxxxx, 8'b1xxxxxxx: Y = 3'b001;
  8'b00000100, 8'b000011xx, 8'b0001xxx, 8'b001xxxxx, 8'b01xxxxxx, 8'b1xxxxxxx: Y = 3'b010;
  8'b00001000, 8'b00011xxx, 8'b001xxxxx, 8'b01xxxxxx, 8'b1xxxxxxx: Y = 3'b011;
  8'b00010000, 8'b001xxxxx, 8'b01xxxxxx, 8'b1xxxxxxx: Y = 3'b100;
  8'b00100000, 8'b01xxxxxx, 8'b1xxxxxxx: Y = 3'b101;
  8'b01000000, 8'b1xxxxxxx: Y = 3'b110;
  8'b10000000: Y = 3'b111;

  default: Y = 3'b000; // Default case for no valid input
endcase
end
endmodule

```


TESTBENCH

```


module banana_26_tb;
  reg [7:0] A;
  wire [2:0] Y;
  wire valid;
  banana_26 dut(A, Y, valid);
  initial begin
    // Apply test cases
    A = 8'b00000000; #10;
    A = 8'b00000001; #10;
    A = 8'b00000010; #10;
    A = 8'b00000100; #10;
    A = 8'b00001000; #10;
    A = 8'b00010000; #10;
    A = 8'b00100000; #10;
    A = 8'b01000000; #10;
    A = 8'b10000000; #10;
    A = 8'b11111111; #10;
    $stop;
  end
endmodule

```



WAVEFORM

 

RTL

 

Technology schematic

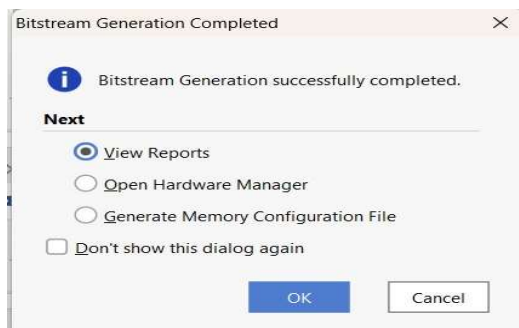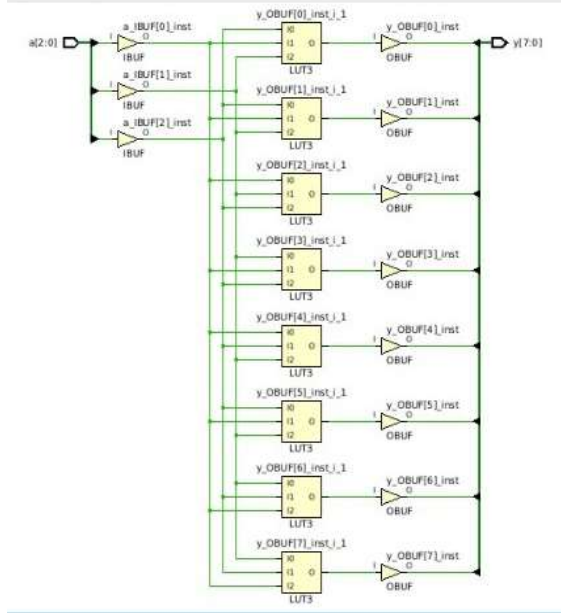

(g) A 3:8 decoder.

CODE

```
module job_q_2.7(input logic [2:0] a, output logic [7:0] y);
  always_comb
  case(a)
    3'b000 : y = 8'b00000001;
    3'b001 : y = 8'b00000010;
    3'b010 : y = 8'b00000100;
    3'b011 : y = 8'b00001000;
    3'b100 : y = 8'b00010000;
    3'b101 : y = 8'b00100000;
    3'b110 : y = 8'b01000000;
    3'b111 : y = 8'b10000000;
    default: y = 8'bxxxxxxxx;
  endcase
endmodule
```

TESTBENCH



```
module job_q_2.7_tb;

  logic [2:0] a;
  logic [7:0] y;



  job_q_2.7 dut (a, y);
```

```
initial begin
    a = 3'b000; #10;
    a = 3'b001; #10;
    a = 3'b010; #10;
    a = 3'b011; #10;
    a = 3'b100; #10;
    a = 3'b101; #10;
    a = 3'b110; #10;
    a = 3'b111; #10;
end
endmodule
```

WAVEFORM

  **RTL**

Technology schematic

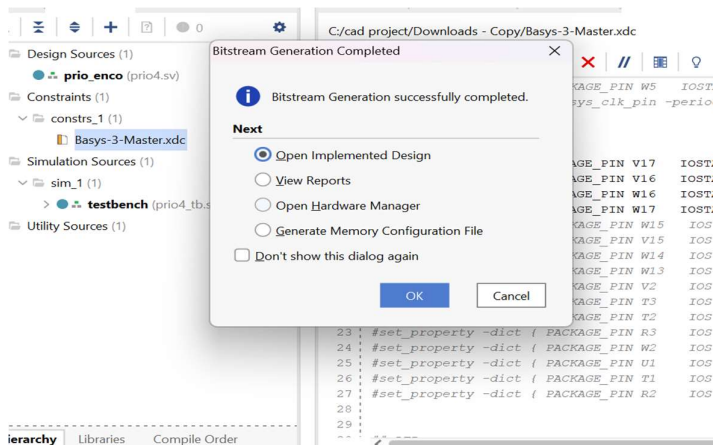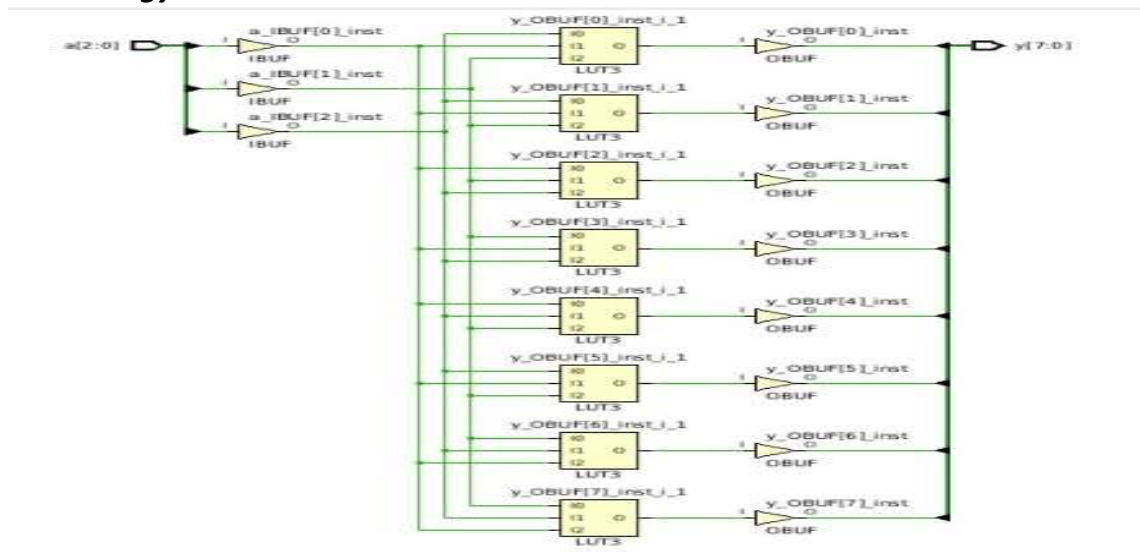

(h) A 4-bit carry propagate adder (with no carry in or out).


CODE

```
module job_q_2.8(  
    input [3:0] A,  
    input [3:0] B,  
    output [3:0] Sum  
);  
    assign Sum = A + B;  
endmodule
```


TESTBENCH

```
module job_q_2.8_tb;  
    reg [3:0] A, B;  
    wire [3:0] Sum;  
  
    carry_job_q_2.8 dut (  
        .A(A),  
        .B(B),  
        .Sum(Sum)  
    );  
  
    initial begin  
        A = 4'b0000; B = 4'b0000; #10;  
        A = 4'b0001; B = 4'b0001; #10;  
        A = 4'b0010; B = 4'b0010; #10;  
        A = 4'b0100; B = 4'b0100; #10;  
        A = 4'b1000; B = 4'b1000; #10;  
        A = 4'b1111; B = 4'b1111; #10;  
        A = 4'b1101; B = 4'b1011; #10;  
        A = 4'b0110; B = 4'b0111; #10;  
        $finish;  
    end  
endmodule
```



WAVEFORM

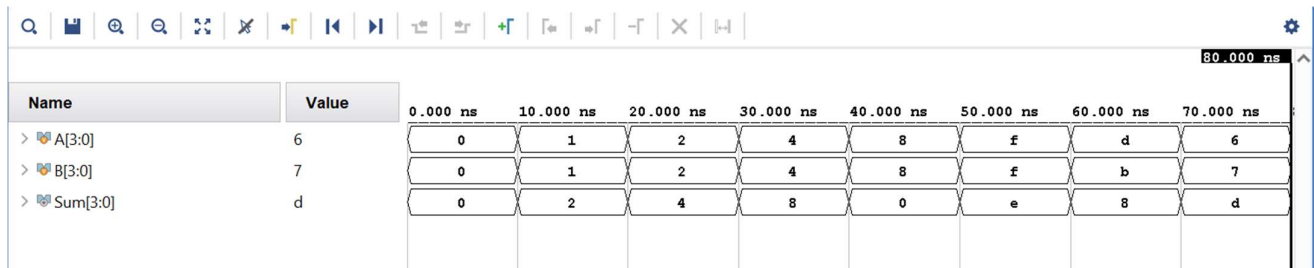


RTL

 

Technology schematic

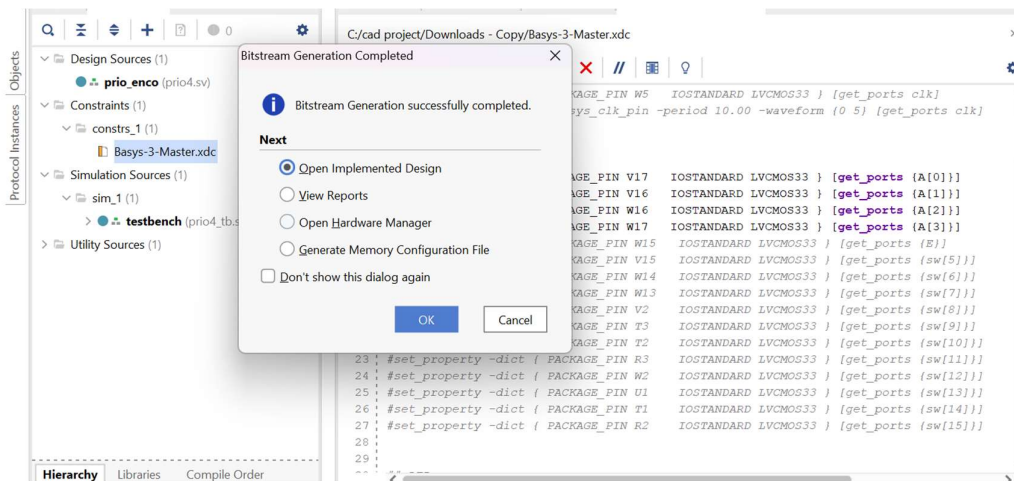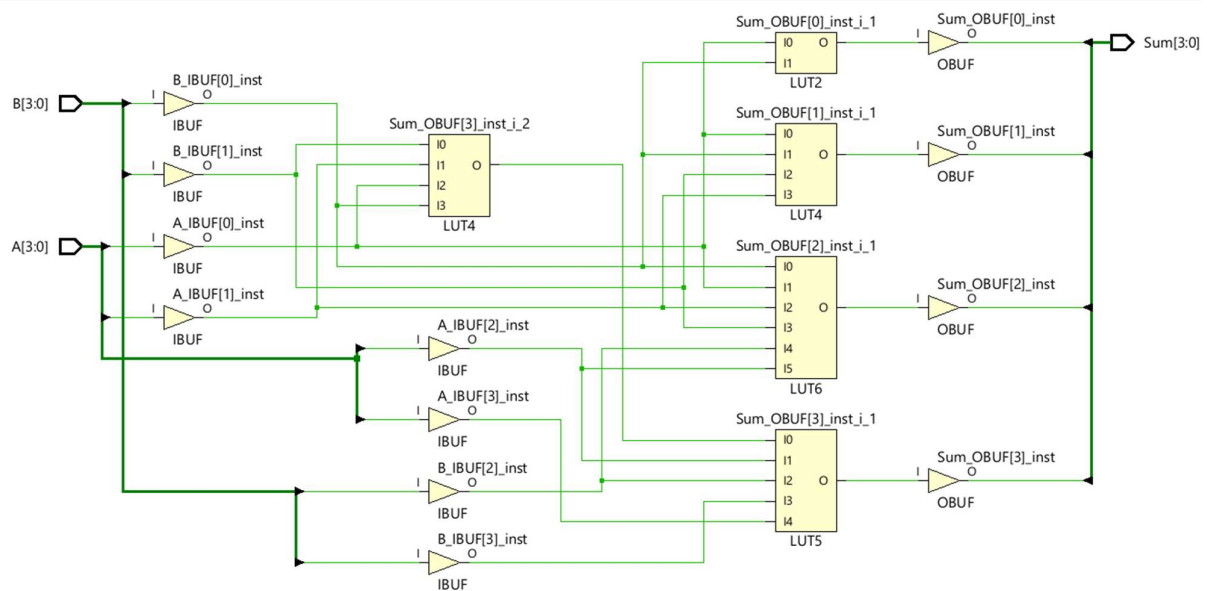

(i) The FSM

 

CODE

```

module job_q_2.9(
    input logic clk,
    input logic reset,
    input logic A,
    input logic B,
    output logic Q
);
    typedef enum logic [1:0] {S0 = 2'b00, S1 = 2'b01, S2 = 2'b10} state_t;
    state_t state, next_state;

```



```

always_ff @(posedge clk or posedge reset) begin
  if (reset)
    state <= S0;
  else
    state <= next_state;
end
always_ff @(state or A or B) begin
  case (state)
    S0:
      if (~A) next_state = S0;
      else next_state = S1;
    S1:
      if (~B) next_state = S1;
      else next_state = S2;
    S2:
      if (~A) next_state = S2;
      else next_state = S0;
      default: next_state = S0;
  endcase
end
assign Q = (state == S2);
endmodule


```

```


TESTBENCH
module job_q_2.9_tb;
reg clk,reset,A,B;
wire Q;
job_q_2.9 dut(.clk(clk),.reset(reset),.A(A),.B(B),.Q(Q));
always #5 clk=~clk;
initial begin
  clk=0;reset=0;A=0;B=0;
  #10 reset=1;#10 reset=0;
  #10 A=1;B=0;#10 A=0;B=0;
  #10 A=0;B=1;#10 A=0;B=0;
  #10 A=1;B=0;#10 A=0;B=0;
  #10 reset=1;#10 reset=0;
  #10 $finish;
end
endmodule

```



WAVEFORM

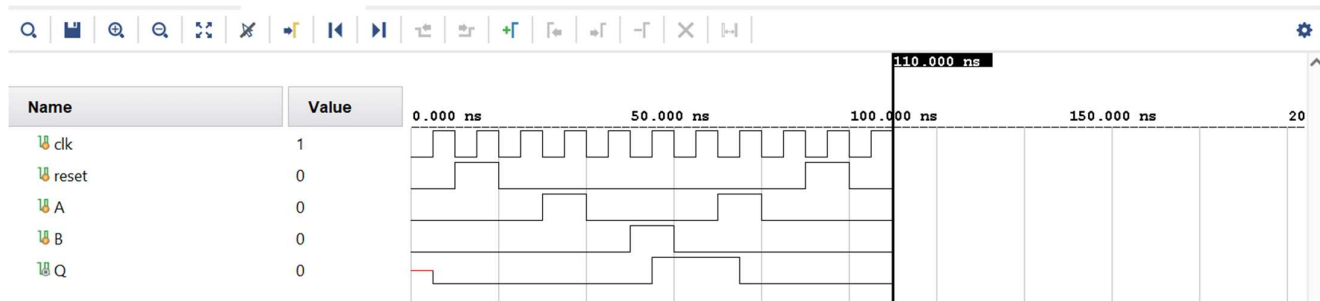

RTL

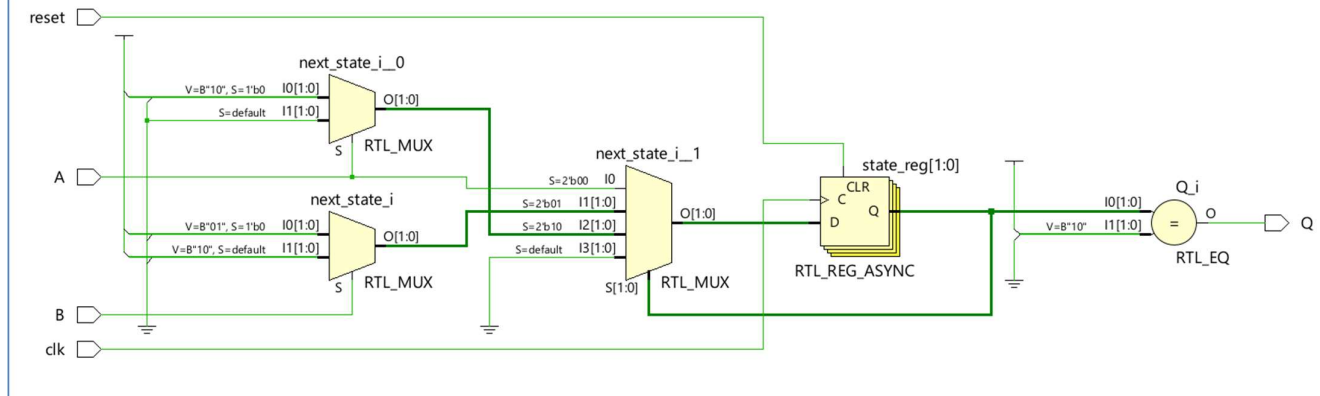

Technology schematic

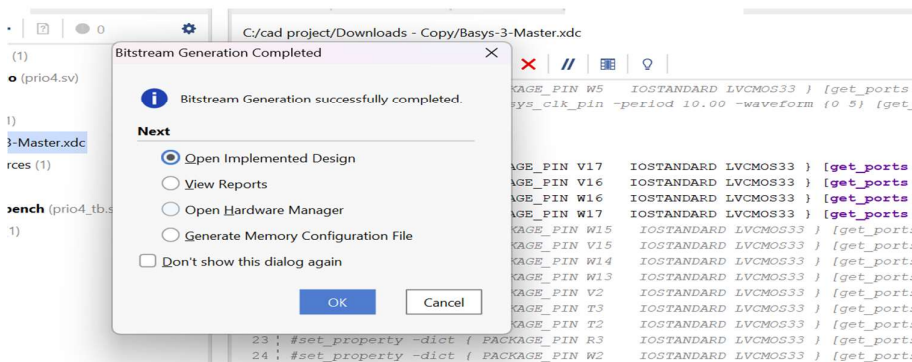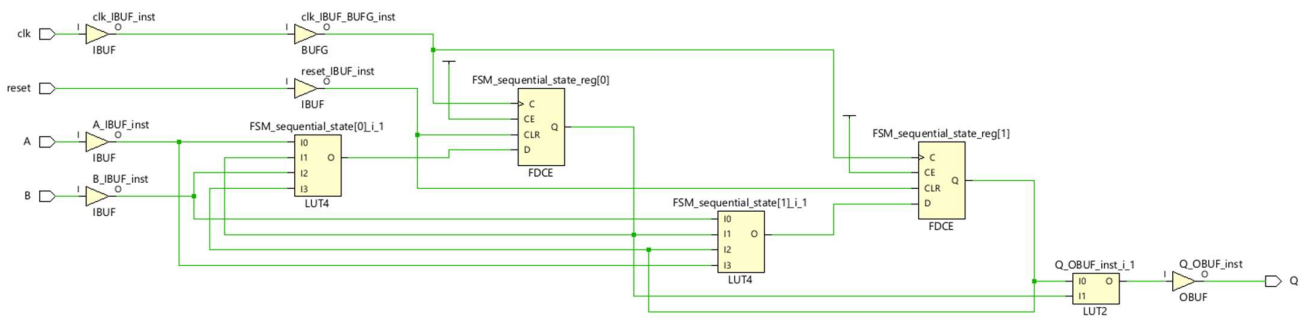

(j) The Gray code counter

CODE

```
module job_q2_10(
    input logic [3:0] B,
    output logic [3:0] G
);
    assign G[3] = B[3];
    assign G[2] = B[3] ^ B[2];
    assign G[1] = B[2] ^ B[1];
    assign G[0] = B[1] ^ B[0];
endmodule
```

TESTBENCH


```
module job_q_2.10_tb ();
    logic [3:0] B;
    logic [3:0] G;
    job_q_2.10 dut (
        .B(B),
```

```


.G(G)
);
initial begin
    B = 4'b0000; #10;
    B = 4'b0001; #10;
    B = 4'b0010; #10;
    B = 4'b0011; #10;
    B = 4'b0100; #10;
    B = 4'b0101; #10;
    B = 4'b0110; #10;
    B = 4'b0111; #10;
    B = 4'b1000; #10;
    B = 4'b1001; #10;
    $finish;
end
endmodule

```

WAVEFORM

 

RTL

 

Technology schematic

